

Ex 17.6

Power



$$V = 50V$$

Nichrome

$$R = 8\Omega$$

$$I = ?$$

$$P = ?$$

$$V = IR$$

$$I = \frac{V}{R} = \frac{50V}{8\Omega} = \boxed{6.25 \frac{V}{\Omega} = \text{Amps}}$$

$$P = IV = 6.25 \text{ Amps} \cdot 50 = \boxed{313 \text{ Watts}}$$

If doubled ( $\times 2$ ) V

$$100V$$

$$I = \frac{100}{8} = \underline{12.5 \text{ Amp}} \text{ doubled}$$

$$P = \frac{V^2}{R} = \frac{100^2}{8} = 1250 \text{ Watts quadrupled}$$

$$P = IV = I^2R = \frac{V^2}{R}$$

$$\frac{Q}{t} \cdot V = IV = P$$

$$\frac{C}{s} \cdot V = \text{Amp} \cdot V = \text{Watt}$$

$$1 \text{ kWh} = 3.6 \times 10^6 \text{ J}$$

← Ohm's Law