


## Chapter 18

### Direct Current Circuits

A source that maintains a current in a closed circuit is called an emf or “charge pump”. A common source is a battery. These sources provide voltage or electric potential measured in volts.

Within a circuit, resistors can be arranged in series or parallel.

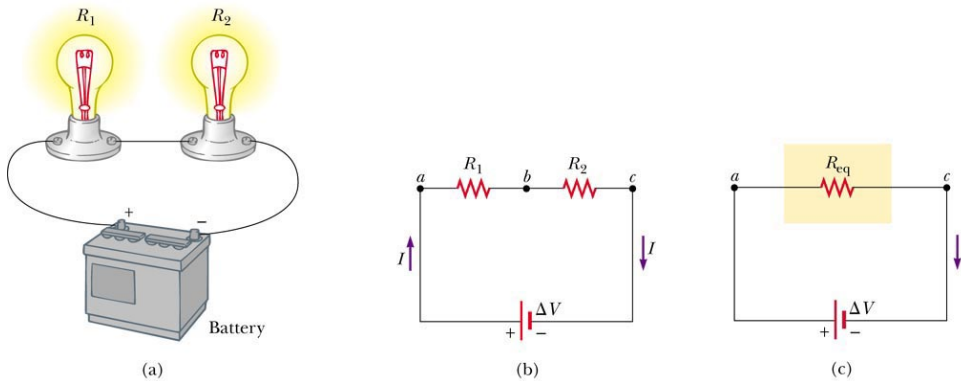In **series**, the current is the same in all the resistors.




© 2003 Thomson - Brooks Cole

The equivalent resistance of a series combination of resistors is the algebraic sum of the individual resistors.

$$R_{eq} = R_1 + R_2 + \dots$$


**V=IR across each one**

$$I_1 = I_2 = I_3 \dots$$

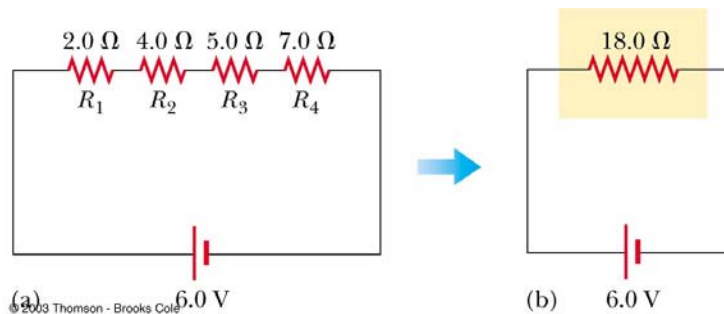

© 2003 Thomson - Brooks Cole

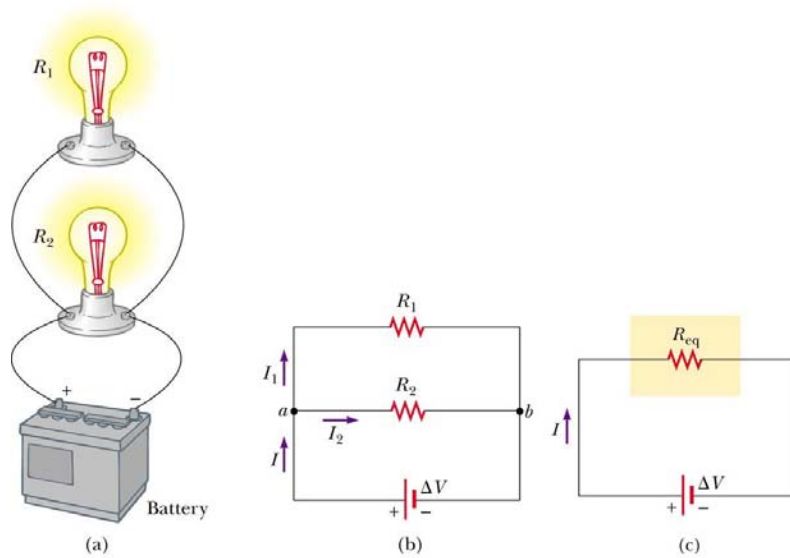
In **parallel**, the current branches depending on the resistance in the branch. The inverse of the equivalent resistance of a parallel branch is the inverse of the algebraic sum of the individual resistances.



$$1/R_{eq} = 1/R_1 + 1/R_2 + \dots$$

$$V_1 = V_2 = \dots$$

$I = V/R$  for each branch

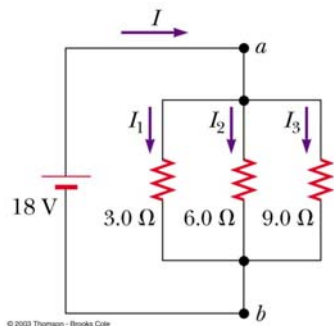

Combination circuits with series and parallel resistors:

