
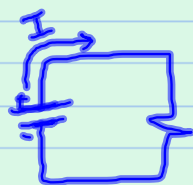


CH18 DC Circuits

Ex. 18.1 p 559

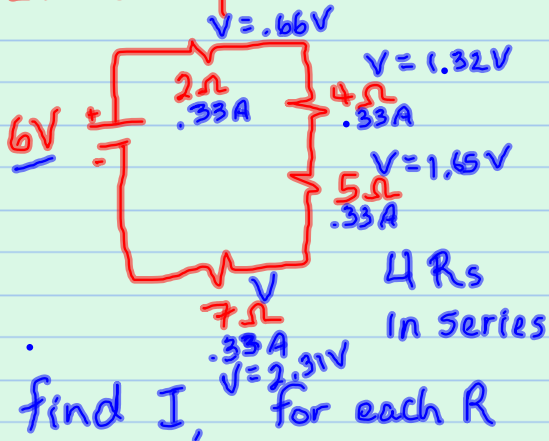

$$R_{eq} = 2 + 4 + 5 + 7 = 18 \Omega$$

$$V = I \cdot R$$

$$I = \frac{V}{R} = \frac{6}{18} = .33A$$

$$V = IR = .33() =$$

\mathcal{E} - electromotive force
emf
ex. battery, generators

R (load) - bulbs, computer

R in series

$$R_{eq} = R_1 + R_2 + \dots$$

$$V_{eq} = V_1 + V_2 + V_3 \dots$$

$$I_1 = I_2 = I_3$$

① find R_{eq}

② find I

$$V = IR$$

③ find V